

Problem assignment on discrete time system realisations (Solutions)


Problem 1

$$y(n] = y[n-1] - \frac{1}{2}y[n-2] + x[n] - x[n-1] + x[n-2] \Rightarrow$$


$$\Rightarrow Y(z) \left(1 - z^{-1} + \frac{1}{2}z^{-2} \right) = X(z) \cdot (1 - z^{-1} + z^{-2}) \Rightarrow$$

$$\Rightarrow H(z) = \frac{1 - z^{-1} + z^{-2}}{1 - z^{-1} + \frac{1}{2}z^{-2}}$$

DIRECT I

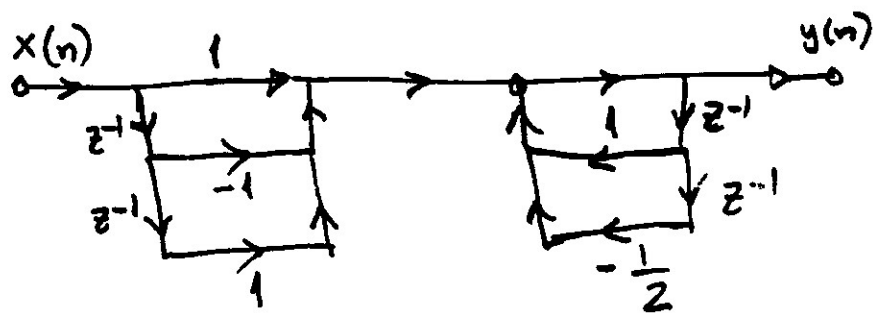

DIRECT II, Cascade, Parallel

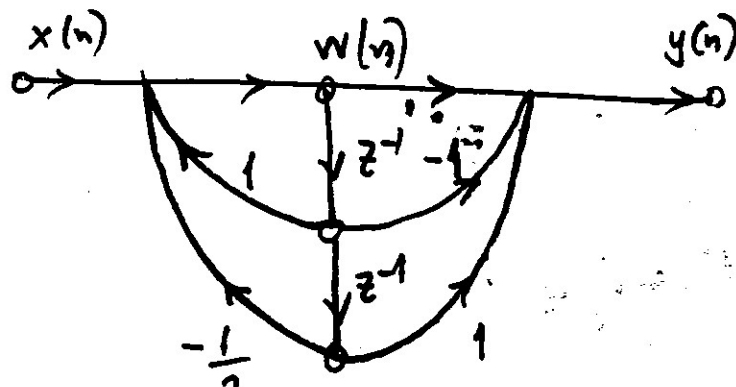

Pr. 2

Determine the cascade and parallel realizations for the system described by the system function

$$H(z) = \frac{10(1 - \frac{1}{2}z^{-1})(1 - \frac{2}{3}z^{-1})(1 + 2z^{-1})}{(1 - \frac{3}{4}z^{-1})(1 - \frac{1}{3}z^{-1})[1 - (\frac{1}{2} + j\frac{1}{2})z^{-1}][1 - (\frac{1}{2} - j\frac{1}{2})z^{-1}]}$$

Solution: The cascade realization is easily obtained from this form. One possible pairing of poles and zeros is

$$H_1(z) = \frac{1 - \frac{2}{3}z^{-1}}{1 - \frac{7}{8}z^{-1} + \frac{3}{32}z^{-2}}$$

$$H_2(z) = \frac{1 + \frac{3}{2}z^{-1} - z^{-2}}{1 - z^{-1} + \frac{1}{2}z^{-2}}$$

and hence

$$H(z) = 10H_1(z)H_2(z)$$


The cascade realization is depicted in Fig. 7.23a.

To obtain the parallel-form realization, $H(z)$ must be expanded in partial fractions. Thus we have

$$H(z) = \frac{A_1}{1 - \frac{3}{4}z^{-1}} + \frac{A_2}{1 - \frac{1}{3}z^{-1}} + \frac{A_3}{1 - (\frac{1}{2} + j\frac{1}{2})z^{-1}} + \frac{A_3^*}{1 - (\frac{1}{2} - j\frac{1}{2})z^{-1}}$$


where A_1, A_2, A_3 , and A_3^* are to be determined. After some arithmetic we find that
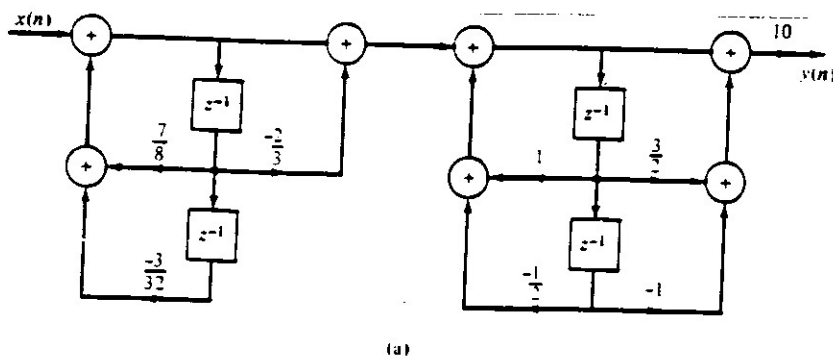
$$A_1 = 2.93, \quad A_2 = -17.68, \quad A_3 = 12.25 - j14.57, \quad A_3^* = 12.25 + j14.57$$




$$\frac{-14.75 - 12.92z^{-1}}{1 - \frac{7}{8}z^{-1} + \frac{3}{32}z^{-2}}$$

$$\frac{24.5 + 26.82z^{-1}}{1 - z^{-1} + \frac{1}{2}z^{-2}}$$

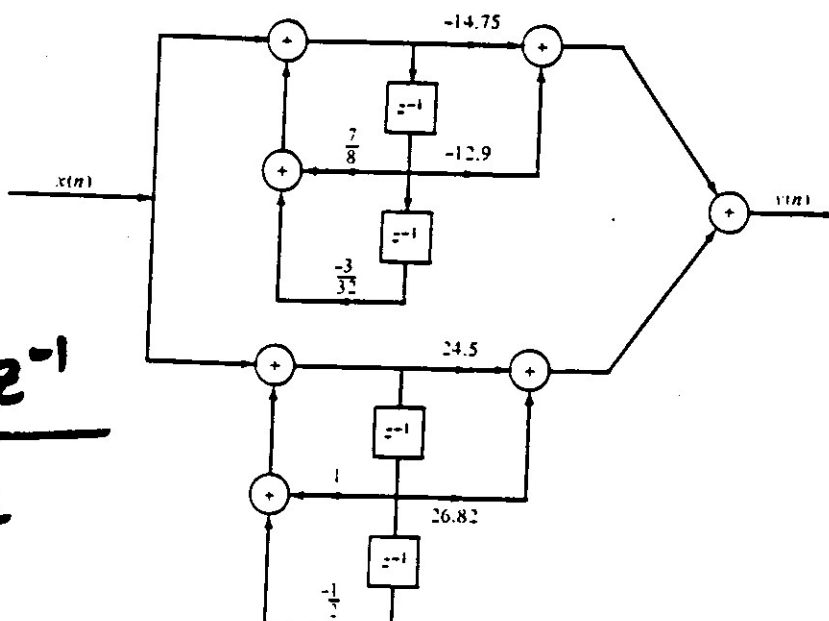

Problem 3

a)

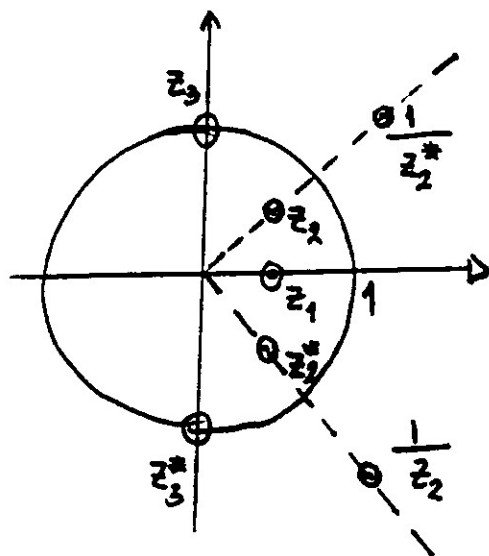

* If a real linear phase FIR Filter has a zero at $z=z_2$ then it also has zeros at $z=\frac{1}{z_2}$, z_2^* , $\frac{1}{z_2^*}$

* If a complex linear phase FIR filter has a zero at $z=z_2$ it also has a zero at $z=\frac{1}{z_2}$

$$b) H(z) = z^{-5} \cdot (z-0.5) \cdot (z-j) \cdot (z+j) \cdot [1-(0.5-j0.5)z^{-1}] \cdot [1-(0.5+j0.5)z^{-1}] \cdot [1-(0.5-j0.5)z] \cdot [1-(0.5+j0.5)z] =$$

$$= z^{-5} \cdot (z-0.5)(z^2+1) (0.5z^2 - 1.5z + 2.25 - 1.5z^{-1} + 0.5z^{-2}) =$$

$$= \underbrace{(1-0.5z^{-1})}_{\text{First-order non-linear phase FIR}} \underbrace{(1+z^{-2})}_{\text{Second-order linear phase FIR}} \underbrace{(0.5-1.5z^{-1}+2.25z^{-2}-1.5z^{-3}+0.5z^{-4})}_{\text{Fourth-order linear-phase FIR}}$$

